

Balika Vidyapith, Lakhisarai

Class 12 Subject Physics(Unit 04) Date 08 07 2020

Note-Wattless Current is not now in syllabus in session (2020 21)

Power in AC Circuit with L, C, R:

$$E = E_0 \sin \omega t$$

$$I = I_0 \sin (\omega t + \Phi) \quad (\text{where } \Phi \text{ is the phase angle between emf and current})$$

$$\text{Instantaneous Power} = E I$$

$$= E_0 I_0 \sin \omega t \sin (\omega t + \Phi)$$

$$= E_0 I_0 [\sin^2 \omega t \cos \Phi + \sin \omega t \cos \omega t \cos \Phi]$$

If the instantaneous power is assumed to be constant for an infinitesimally small time dt , then the work done is

$$dW = E_0 I_0 [\sin^2 \omega t \cos \Phi + \sin \omega t \cos \omega t \cos \Phi]$$

Work done over a complete cycle is

$$W = \int_0^T E_0 I_0 [\sin^2 \omega t \cos \Phi + \sin \omega t \cos \omega t \cos \Phi] dt$$

$$W = E_0 I_0 \cos \Phi \times T / 2$$

Average Power over a cycle is $P_{av} = W / T$

$$P_{av} = (E_0 I_0 / 2) \cos \Phi$$

(where $\cos \Phi = R / Z$)

$$P_{av} = (E_0 / \sqrt{2}) (I_0 / \sqrt{2}) \cos \Phi$$

$$= R / \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$

is called Power Factor)

$$P_{av} = E_v I_v \cos \Phi$$

$$P_{av} = E_v I_v \cos \Phi$$

Power in AC Circuit with R:

In R, current and emf are in phase.

$$\Phi = 0^\circ$$

$$P_{av} = E_v I_v \cos \Phi = E_v I_v \cos 0^\circ = E_v I_v$$

Power in AC Circuit with L:

In L, current lags behind emf by $\pi/2$.

$$\Phi = -\pi/2$$

$$P_{av} = E_v I_v \cos (-\pi/2) = E_v I_v (0) = 0$$

Power in AC Circuit with C:

In C, current leads emf by $\pi/2$.


$$\Phi = +\pi/2$$

$$P_{av} = E_v I_v \cos (\pi/2) = E_v I_v (0) = 0$$

Note:

Power (Energy) is not dissipated in Inductor and Capacitor and hence they find a lot of practical applications and in devices using alternating current.

Wattless Current or Idle Current:

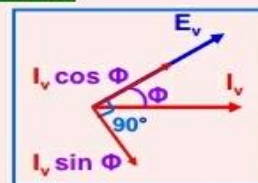

The component $I_v \cos \Phi$ generates power with E_v .

However, the component $I_v \sin \Phi$ does not contribute to power along E_v and hence power generated is zero. This component of current is called wattless or idle current.

$$P = E_v I_v \sin \Phi \cos 90^\circ = 0$$

