

VIDYA BHAVAN, BALIKA VIDYAPEETH
SHAKTI UTTAN ASHRAM, LAKHISARAI, PIN:-811311

SUBJECT:- PHYSICS

CLASS:- XTH

DATE:- 13/05/XXI

SUBJECT TEACHER:- MR. NEEL NIRANJAN

CHAPTER 1. (ELECTRICITY) (BASED ON NCERT PATTERN) (IMPORTANT QUESTIONS)

Q1. How many 176Ω resistors (in parallel) are required to carry 5 A on a 220 V line?

Ans. $I = 5 \text{ A}$, $V = 220 \text{ V}$

Let the number of 176Ω resistors be n .

$$\frac{1}{R_p} = \frac{1}{176} + \frac{1}{176} \dots + n$$

$$\frac{1}{R_p} = \frac{n}{176} \text{ or } R_p = \frac{176}{n}$$

$$\text{As } R = \frac{V}{I}$$

$$\frac{176}{n} = \frac{220}{5}$$

$$n = \frac{176 \times 5}{220} = 4$$

Hence, four resistors of 176Ω are required to carry 5 A on a 220 V line.

Q2. show how you would connect three resistors each of resistance 6Ω , so that the combination has a resistance of (i) 9Ω , (ii) 4Ω .

Ans. (i) To get 9Ω connect 2 resistors of 6Ω in parallel and 3rd resistor in series.

$$\frac{1}{R_p} = \frac{1}{6} + \frac{1}{6} = \frac{2}{6} = \frac{1}{3}$$

$$R_p = 3 \Omega$$

$$R_{\text{total}} = R_p + R$$

$$= 3 + 6 = 9 \Omega$$

(ii) To get 4Ω – Connect 2 resistors in series and the third in parallel to both of them

$$R_s = 6 + 6 = 12 \Omega$$

$$\frac{1}{R_{\text{total}}} = \frac{1}{R_s} + \frac{1}{R}$$

$$= \frac{1}{12} + \frac{1}{6} = \frac{1+2}{12} = \frac{1}{4}$$

$$R_{\text{total}} = 4 \Omega$$

Q3. Several electric bulbs designed to be used on a 220 V electric supply line, are rated 10 W. How many lamps can be connected in parallel to each other across (the two wires) of a 220 V line if the maximum allowable current is 5 A?

Ans. $P = 10 \text{ W}$

$$V = 220 \text{ V}$$

$$I = ?$$

$$\text{Using, } I = \frac{P}{V}$$

$$= \frac{10}{220} = \frac{1}{22}$$

If number of bulbs connected to current of 5 A is n . Then,

$$\frac{1}{22} n = 5$$

$$n = 5 \times 22 = 110$$

110 bulbs can be attached