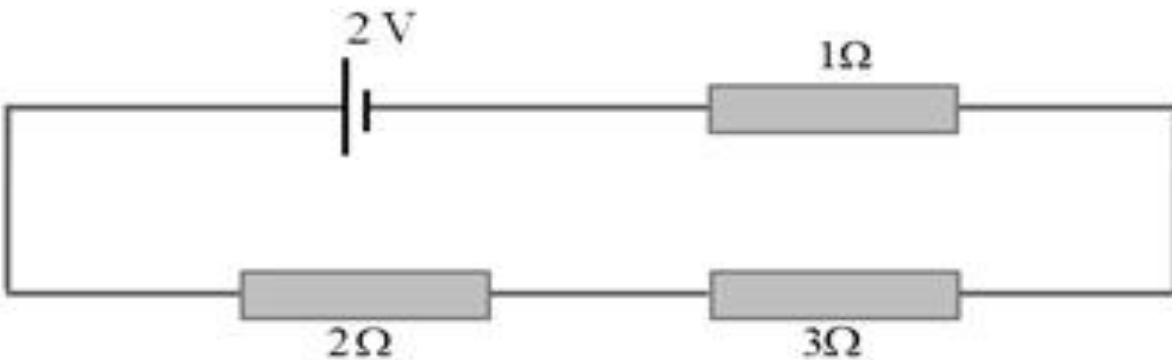


CHAPTER 1. (ELECTRICITY REVISION) (BASED ON NCERT PATTERN)


1. The potential difference across the $3\ \Omega$ resistor in the following diagram is:



- (a) $1/9\ \text{V}$
- (b) $1/2\ \text{V}$
- (c) $2\ \text{V}$
- (d) $1\ \text{V}$

Answer: (d) $1\ \text{V}$

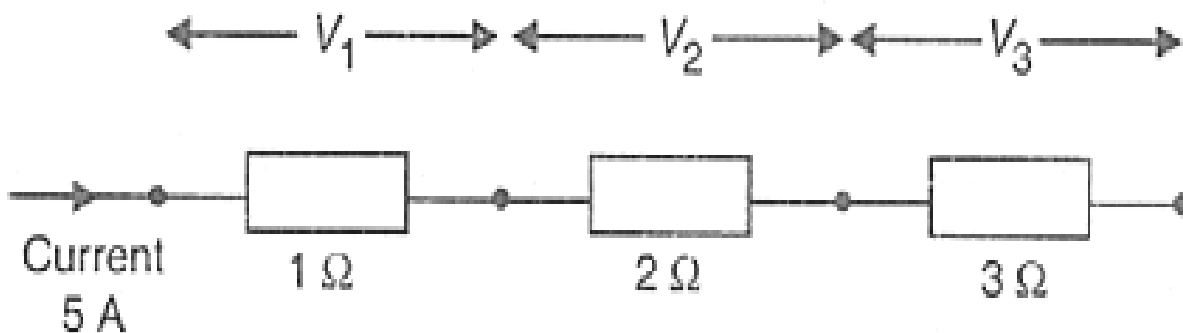2. V_1 , V_2 and V_3 are the potential differences across the $1\ \Omega$, $2\ \Omega$ and $3\ \Omega$ resistors in the following diagram, and the current is $5\ \text{A}$.



Which of the following shows the correct values of V_1 , V_2 and V_3 measured in volts?

- (a) $V_1 = 1$, $V_2 = 2$ and $V_3 = 3$
- (b) $V_1 = 5$, $V_2 = 10$ and $V_3 = 15$
- (c) $V_1 = 5$, $V_2 = 2.5$ and $V_3 = 1.6$
- (d) $V_1 = 4$, $V_2 = 3$ and $V_3 = 2$

Answer: (b) $V_1 = 5$, $V_2 = 10$ and $V_3 = 15$

3. A wire of resistance R_1 is cut into five equal pieces. These five pieces of wire are then connected in parallel. If the resultant resistance of this combination be R_2 , then the ratio R_1/R_2 is:

- (a) $1/25$
- (b) $1/5$
- (c) 5
- (d) 25

Answer: (d) 25

4. Two appliances of rating 200 watt-250 volts and 100 watt-250 volts are joined in series to a 250 volts supply. Total power consumed in the circuit is

- (a) 46 watt
- (b) 67 watt
- (c) 10 watt
- (d) 30 watt

Answer: (b) 67 watt

5. When a current 'I' flows through a resistance 'R' for time 't' the electrical energy spent is given by

- (a) IRt
- (b) I^2Rt
- (c) IR^2t
- (d) I^2R/t

Answer: (b) I^2Rt

