

VIDYA BHAVAN, BALIKA VIDYAPEETH
SHAKTI UTTHAN ASHRAM, LAKHISARAI, PIN:-811311

SUBJECT:- PHYSICS

CLASS:- XTH

DATE:26/07/XX

SUBJECT TEACHER:- MR. NEEL NIRANJAN

CHAPTER 1. (ELECTRICITY REVISION) (BASED ON NCERT PATTERN)

1. To get 2Ω resistance using only 6Ω resistors, the number of them required is

- (a) 2 (b) 3
(c) 4 (d) 6


2. Two devices are connected between two points say A and B in parallel. The physical quantity that will remain the same between the two points is

- (a) current (b) voltage
(c) resistance (d) None of these

3. The least resistance obtained by using 2Ω , 4Ω , 1Ω and 100Ω is

- a) $< 100 \Omega$ (b) $< 4 \Omega$
(c) $< 1 \Omega$ (d) $> 2 \Omega$

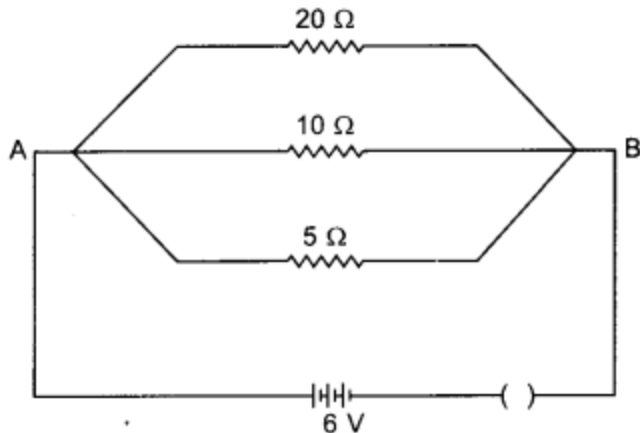4. Calculate the current flows through the 10Ω resistor in the following circuit.



- (a) 1.2 A (b) 0.6 A
(c) 0.2 A (d) 2.0 A